

Section 3.2.4 – Transformers

Transformers

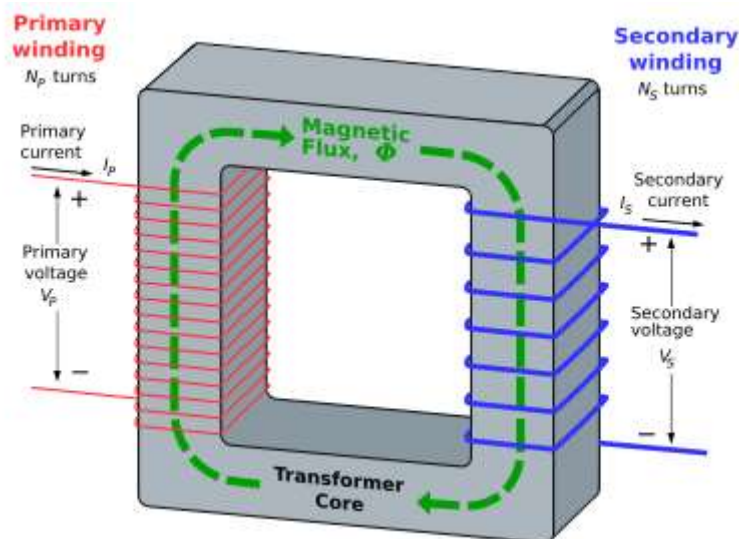


Figure 1

A transformer as shown in **Figure 1** is a device that consists of an **iron core** and an input and output, or rather a **primary coil** and a **secondary coil**. When an **AC voltage** is applied to the primary coil an **alternating magnetic field** is established within the **iron core**. This in turn will induce an **alternating voltage** in the **secondary coil**.

The induced voltage (or current) located at the secondary coil depends upon the:

- input voltage
- number of turns in both the primary and secondary coils

Transformer Equations

$$\frac{V_S}{V_P} = \frac{N_S}{N_P} = \frac{I_P}{I_S}$$

Where V_S = Voltage in the secondary coil
 V_P = Voltage in the primary coil
 N_S = Number of turns in the secondary coil
 N_P = Number of turns in the primary coil
 I_P = Current in the primary coil
 I_S = Current in the secondary coil

An **ideal transformer** would be **100%** efficient. That is all electrical power in is transferred into electrical power out. In reality this isn't the case. Power is lost in:

- both the primary and secondary coils (minor loss)
- eddy currents within the iron core (major loss)

To overcome power loss within the core, they are constructed with alternate layers of iron and insulation. Such transformers are approximately 99% efficient.

Ideally: Power in the primary coil = Power in the secondary coil
 $P_P = P_S$

$$\therefore V_P I_P = V_S I_S$$

Classification

If $V_S > V_P$ Transformer is classified as a “**Step-Up**” transformer
 If $V_S < V_P$ Transformer is classified as a “**Step-Down**” transformer

Example 1

In a particular transformer, the primary coil is wound with 240 coils and the secondary coil is wound with 720 coils. If 24 V AC is connected to the input terminals, calculate the output voltage, assuming no power loss. Classify this transformer as either step-up or step-down.

$N_P = 240$ turns
 $N_S = 720$ turns
 $V_P = 24$ V AC
 $V_S = ?$

$$\frac{V_S}{V_P} = \frac{N_S}{N_P} \quad \therefore V_S = V_P \times \frac{N_S}{N_P}$$

$$V_S = 24 \times \frac{720}{240} \\ = \underline{\underline{72 \text{ V AC}}}$$

As $V_S > V_P$, this is a step-up transformer.

Example 2

A step-up transformer is connected to an AC generator that delivers 120 V and 80 A. The ratio of the number of turns in the secondary to the number of turns in the primary is 500.

- What is the voltage in the secondary coil?
- What is the power input?
- What is the maximum power output?
- What is the maximum current in the secondary coil?

Part A.

$V_P = 120$ V
 $I_P = 80$ A
 $N_S/N_P = 500$
 $V_S = ?$

$$V_S = V_P \times (N_S/N_P) \\ = 120 \times 500 \\ = 60\,000 \text{ V} \\ = \underline{\underline{60 \text{ kV}}}$$

Part B.

$V_P = 120$ V
 $I_P = 80$ A
 $N_S/N_P = 500$
 $P_P = ?$

$$P_P = V_P \times I_P \\ = 120 \times 80 \\ = 9\,600 \text{ W} \\ = \underline{\underline{9.6 \text{ kW}}}$$

Part C.

P_S (max) = ?
 Max. possible power output occurs if transformer is 100% efficient.
 P_S (max) = $P_P = \underline{\underline{9.6 \text{ kW}}}$

Part D.

$$P_S = 9.6 \times 10^3 \text{ W} \quad P_S = V_S \times I_S \\ V_S = 60 \times 10^3 \text{ V} \quad \therefore I_S = \frac{P_S}{V_S} \\ I_S = ? \quad = 9.6 \times 10^3 / 60 \times 10^3 \\ = \underline{\underline{0.16 \text{ A}}}$$

or

$$I_P = 80 \text{ A} \quad I_S/I_P = N_P/N_S \\ N_S/N_P = 500 \quad \therefore I_S = I_P \times N_P/N_S \\ I_S = ? \quad = 80 \times (1/500) \\ = \underline{\underline{0.16 \text{ A}}}$$

Eddy Currents

We already know that an **EMF is induced** when a **change of magnetic flux** occurs. This EMF will be induced in any conductor experiencing a change of flux, whether it is intended or not. The current that this EMF produces is called an **eddy current**.

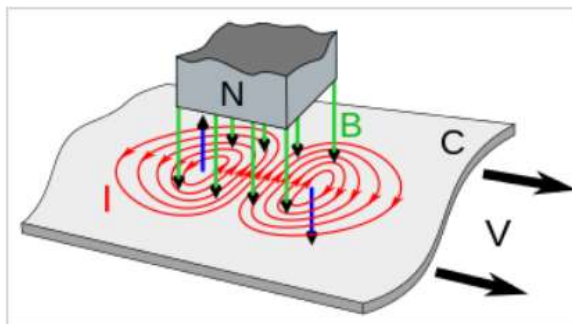


Figure 2

Eddy currents (I , red) induced in a conductive metal plate (C) as it moves to right under a magnet (N). The magnetic field (B , green) is directed down through the plate, as shown in **Figure 2**.

The increasing field at the leading edge of the magnet (left) **induces a counterclockwise current**, which by Lenz's law creates its own **magnetic field (left blue arrow) directed up**, which opposes the magnet's field, producing a retarding force.

Similarly, at the trailing edge of the magnet (right), a **clockwise current and downward counterfield** is created (right blue arrow) also producing a retarding force.

Eddy currents can cause **heating** in the **soft iron core** of a transformer. To overcome this, transformers are often made of **thin layers of soft iron** separated by **insulated layers**, as shown in **Figure 3**. This reduces the build-up of eddy currents and reduces the heating effect within the transformer.

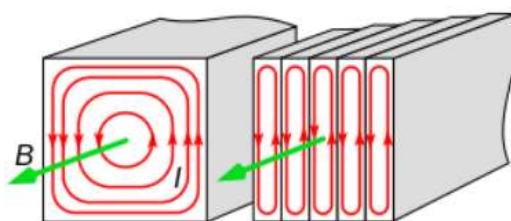



Figure 3

Exam Style Questions

Questions 1 to 4 relate to the following information

A student is investigating the operation of a transformer she has built using some wire coils and a soft iron rod. The diagram below shows her experimental set up.

Coil 1 has 10 loops and **Coil 2** has 20 loops.

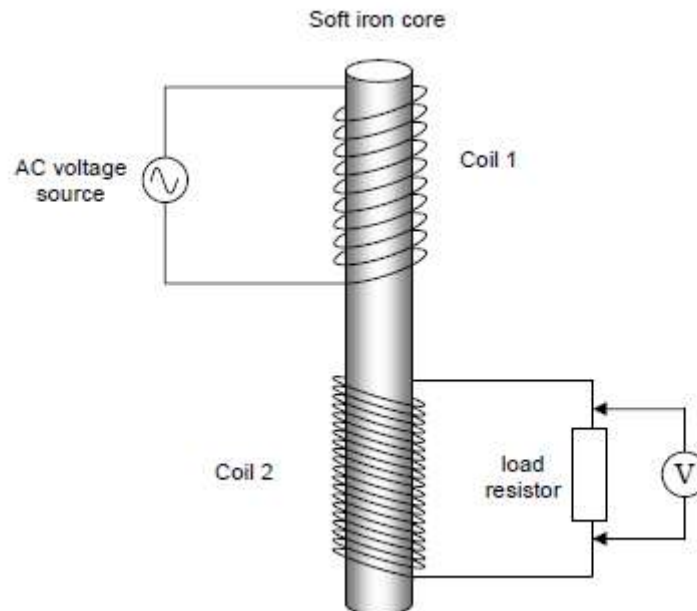

Question 1.

The AC voltage source supplies 20 V into Coil 1.

Calculate the reading on the voltmeter across the load resistor in Coil 2?

$$\begin{aligned}
 V_2 &= ? \\
 V_1 &= 20 \text{ V} \\
 N_2 &= 20 \text{ loops} \\
 N_1 &= 10 \text{ loops} \\
 \frac{V_2}{V_1} &= \frac{N_2}{N_1} \\
 \therefore V_2 &= V_1 \times \frac{N_2}{N_1} \\
 &= 20 \times \frac{20}{10} \\
 &= 40 \text{ Volts}
 \end{aligned}$$

40 V

What is the major assumption you have made in this calculation?

Assumption:

That her transformer is “ideal” or that the power in the first coil ($P_{\text{coil 1}}$) is equal to the power in the second coil ($P_{\text{coil 2}}$)

Question 2.

Explain the purpose of the soft iron core in this experiment.

The soft iron core links the two coils magnetically, OR
It carries the magnetic field from coil 1 to coil 2

Questions 3 and 4 require the following further information

In a further experiment the input voltage from the power supply is altered and the voltage across the load resistor is now measured to be 50 V. The load resistor is 560 Ω .

Question 3.

What is the power being consumed by the load resistor?

$$\begin{aligned}
 P &= ? \\
 V_2 &= 50 \text{ V} \\
 R &= 560 \Omega \\
 P &= \frac{V^2}{R} \\
 \therefore P &= \frac{50^2}{560} \\
 &= 4.46 \text{ Watts}
 \end{aligned}$$

4.46 W

Question 4.

What is the current running through the power supply?

$$\begin{aligned}
 I_1 &= ? \\
 I_2 &= 0.09 \text{ A} \\
 N_1 &= 10 \text{ loops} \\
 N_2 &= 20 \text{ loops} \\
 I_2 &= \frac{P_2}{V_2} \\
 \therefore I_2 &= \frac{4.46}{50} \\
 &= 0.09 \text{ A}
 \end{aligned}$$

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = \frac{I_p}{I_s}$$

$$\therefore \frac{I_2}{I_1} = \frac{N_2}{N_1}$$


$$\begin{aligned}
 \therefore I_2 &= I_1 \times \frac{N_2}{N_1} \\
 &= 0.09 \times \frac{20}{10} \\
 &= 0.18 \text{ A}
 \end{aligned}$$

0.18 A

Questions 5 and 6 refer to the following information

A student is investigating the operation of a transformer she has built using some wire coils and a soft iron rod. The diagram below shows her experimental set up.

Coil 1 has 10 loops and **Coil 2** has 20 loops.

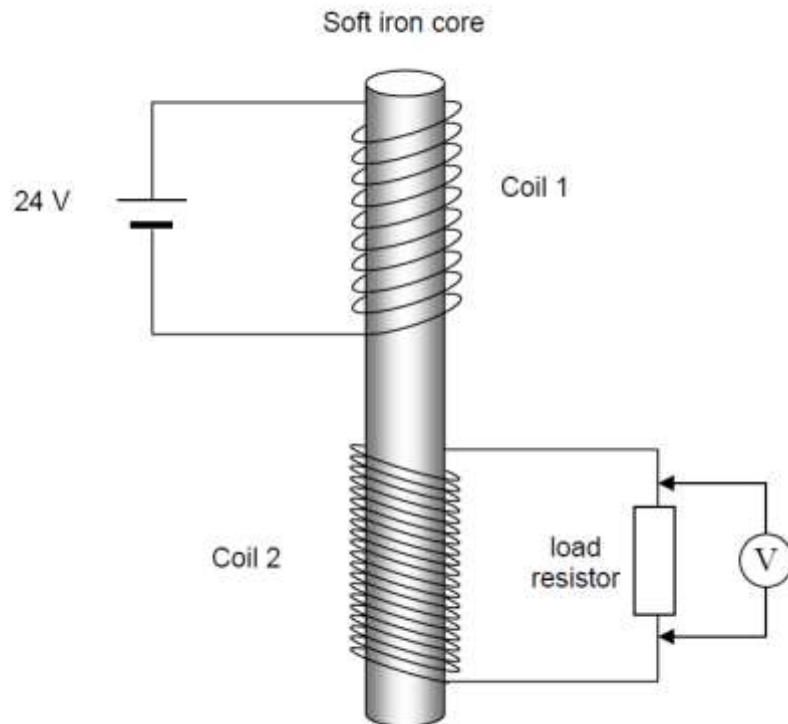

Question 5.

What is the reading on the voltmeter across the load resistor in **Coil 2**?

0 V

Explain your answer:

No voltage is produced if DC is supplied to coil 1. To operate properly a transformer needs a changing voltage in the primary coil to produce a changing flux hence inducing a voltage in the secondary coil.

Question 6.

Give one change that will cause a higher voltage to be induced in coil 2

- Change the supply to coil 1 to AC

Give one other change that would further increase the voltage induced in coil 2.

- Increase the number of coils in coil 2
- Decrease the number of coils in coil 1
- Increase the 24 V supply to coil 1